



TECHNISCHE
UNIVERSITÄT
DRESDEN

Faculty of Computer Science Institute of Computer Engineering, Chair of VLSI Design, Diagnostics & Architecture

VHDL – SEQUENTIAL LOGIC DESCRIPTION

Dr. Thomas B. Preußner

thomas.preusser@tu-dresden.de

Dresden, July 4, 2014



Goals of this Lecture

- Show how sequential logic is modeled.
- Give examples for standard structures:
 - Plain registers,
 - Counters, and
 - State machines.

Covered Scope

- Sequential logic has *state*.
- We address *synchronous* sequential logic where state changes occur upon active clock edges.
- An *asynchronous* reset or set signal may be present (but its use is discouraged).

Basic Approach

Use a **process**, which is triggered by an event on:

- the clock input, or
- one of the asynchronous controls.

```
process(clk, rst) — !!!: ONLY inputs that may  
begin — induce a state transition  
    if rst = '1' then — asynchronous reset  
        Q <= '0';  
    elsif clk'event and clk = '1' then — positive clock edge  
        Q <= D;  
    end if;  
end process;
```

Fully Synchronous Design

```
process(clk)           — !!!: ONLY inputs that may
begin                 — induce a state transition
  if clk 'event and clk = '1' then — positive clock edge
    if rst = '1' then           — synchronous reset
      Q <= '0';
    else
      Q <= D;
    end if;
  end if;
end process;
```

The formula `clk 'event and clk = '1'` is often abbreviated by the more sophisticated:

```
function rising_edge(signal s : std_ulogic) return boolean is
begin
  return (s'event and (to_X01(s) = '1') AND (to_X01(s'last_value) = '0'));
end;
```

which can cope with any transition from '0'|'L' => '1'|'H'.


Synthesis tools accept both.

Conditional State Transitions

State transitions may be guarded, as by enable logic, or derived from more complex computations.

 Example: D-FF with an enable and a synchronous reset:

```
process (clk) — !!!: ONLY inputs that may
begin          — induce a state transition
    if rising_edge (clk) then          — positive clock edge
        if rst = '1' then              — synchronous reset
            Q <= '0';
        elsif E = '1' then            — enable
            Q <= D;
        end if;
    end if;
end process;
```



Beware: you *cannot* model combinatorics deriving from the state within the same process.

Permissible Clock

$$f = \frac{1}{T}$$

Proper operation requires:


$$\forall t_{\text{comp}} \cdot t_{\text{clock2output}} + t_{\text{comp}} + t_{\text{setup}} \leq T$$

Synthesis ensures this property or reports an error if it is unable to achieve the specified timing.

This constraint is checked for all FF-FF paths (within the same clock domain). The longest such paths are called the *critical* paths.


What about asynchronous inputs?

Asynchronous Inputs

 

- Input switches at an *arbitrary* time (with respect to the device clock).
- Propagation through the combinatorics by the next active edge is *not* assured.
- Inconsistencies in the system state may arise from different path lengths.

Asynchronous Inputs

 

- Register-register delays are determined by the synthesis tool.
→ A warning is generated if the clock constraint cannot be satisfied.
- Often, there is a second FF-stage for masking meta-stabilities.
- Note that also Reset buttons are asynchronous inputs.

Standard Pattern: Shift Register

For data serialization (here: MSB first):

```
signal Buf           : std_logic_vector(7 downto 0);  
signal Load, Shift : std_logic;  
...  
process(clk)  
begin  
    if rising_edge(clk) then  
        if Load = '1' then  
            Buf <= Dat;  
        elsif Shift = '1' then  
            Buf <= Buf(Buf'left-1 downto 0) & '-';  
        end if;  
    end if;  
end process;
```

Standard Pattern: Shift Register

As ring counter:

```
signal Buf    : std_logic_vector(7 downto 0);  
signal Shift  : std_logic;  
...  
process(clk)  
begin  
  if rising_edge(clk) then  
    if rst = '1' then  
      Buf    <= (others => '0'); — default assignment  
      Buf(0) <= '1';           — override wins  
    elsif Shift = '1' then  
      Buf <= Buf(Buf'left-1 downto 0) & Buf(Buf'left);  
    end if;  
  end if;  
end process;
```

Array Construction

- by aggregate composition: ('0', '0', '0', '1')
 - with positional association: (0 => '0', 1 => '0', 2 => '0', 3 => '1')
 - using ranges: (0 **to** 2 => '0', 3 => '1')
 - simplified (using character literals only): "0001", x"1", 4x"1"
- as slice: a(5 **downto** 2)
- from concatenation: a(7 **downto** 6) & a(3 **downto** 2) & '—'

For assignments:

- only length matters,
- left goes left and right goes right,
- exact index range and direction are irrelevant,
- **others** range may be used on right hand side.

Standard Pattern: Counter

For event counting:

```
signal Cnt    : unsigned(17 downto 0) := (others => '0');  
signal Event  : std_logic;  
...  
process(clk)  
begin  
    if rising_edge(clk) then  
        if rst = '1' then  
            Cnt <= (others => '0');  
        elsif Event = '1' then  
            Cnt <= Cnt + 1;  
        end if;  
    end if;  
end process;
```


Standard Pattern: Counter

As delay counter:

```
signal Cnt : signed(log2ceil(CNT_DELAY-1) downto 0)
           := ('0', others => '-');
signal Init, Done : std_logic;
...
process(clk)
begin
    if rising_edge(clk) then
        if Init = '1' then
            Cnt <= to_signed(CNT_DELAY-2, Cnt'length);
        elsif Shift = '1' then
            Cnt <= Cnt - 1; — Advantage of counting down?
        end if;
    end if;
end process;
Done <= Cnt(Cnt'left);
```



Interface Definition

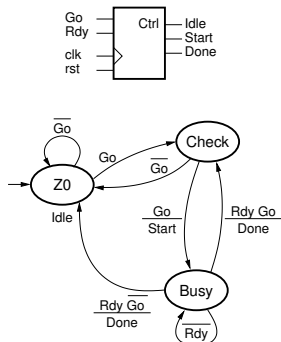



entity ctrl **is**
port(

rst, clk : **in** bit; — *Reset, Clock*
Go : **in** bit; — *Start cycle*
Rdy : **in** bit; — *Stop cycle*

Idle : **out** bit; — *Idle*
Start : **out** bit; — *Start of cycle*
Done : **out** bit — *End of cycle*

);
end ctrl;

SM-Chart

 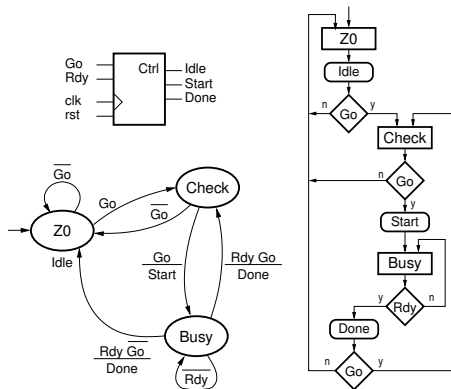

- equivalent to a state diagram,
- precise modeling of hierarchical decisions, and
- easy to translate into an HDL.

Types and Signals

```
architecture rtl of ctrl is  
  type tState is (Z0, Check, Busy);  
  signal State      : tState := Z0; — state register  
  signal NextState : tState;      — combinatorial computation  
begin — of successor state  
  ...  
end rtl;
```

Common Problem:

Initialization of register signals should be equivalent to their reset assignment!

Otherwise inconsistencies between the system states after an initialization (e.g. FPGA-programming) and after a reset are possible. → *Happy Debugging!*

If there is no initialization, synthesis tools try to deduce the initialization state from the reset description – simulators do not!




Registers

```
architecture rtl of strg is
  type tState is (Z0, Check, Busy);
  signal State      : tState := Z0; — state register
  signal NextState : tState;      — combinatorial computation
begin                                — of successor state
  — Sequential Process
  process(clk)
  begin
    if clk'event and clk = '1' then — rising edge
      if rst = '1' then              — synchronous reset
        State <= Z0;
      else
        State <= NextState;
      end if;
    end if;
  end process;

  ...
end rtl;
```

Combinatorics

 

— *Combinatorial Process*

```
process(State, Go, Rdy)
begin
```

— *Default Assignments*

```
NextState <= State;
Idle      <= '0';
Start     <= '0';
Done      <= '0';
```

```
case State is
```

```
  when Z0 =>
```

```
    Idle <= '1';
```

```
    if Go = '1' then
```

```
      NextState <= Check;
```

```
    end if;
```

```
  when Check =>
```

```
    if Go = '0' then
```

```
      NextState <= Z0;
```

```
    else
```

```
      Start <= '1';
```

```
      NextState <= Busy;
```

```
    end if;
```

```
end case;
```

```
end process;
```

```
when Busy =>
```

```
  if Rdy = '1' then
```

```
    Done <= '1';
```

```
    if Go = '0' then
```

```
      NextState <= Z0;
```

```
    else
```

```
      NextState <= Check;
```

```
    end if;
```

```
  end if;
```

— *not required here*

— *completes state enumeration*

```
when others =>
```

```
  null; — does nothing
```

```
end case;
```

```
end process;
```