



Summerschool

Modeling and Designing Dependable Embedded Systems
— Lab 3 —

Problem 1 Consider the two following implementations of the **entity** sigvsvar:

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity sigvsvar is  
end entity;
```

Variant 1:

```
architecture sig of sigvsvar is  
    signal a : std_logic := '0';  
    signal b : std_logic := '1';  
    signal c : std_logic := '0';  
begin  
    process  
    begin  
        wait for 5 ns;  
        c <= a xor b;  
        b <= a xor c;  
        wait for 5 ns;  
        c <= a xor b;  
        b <= a xor c;  
        wait;  
    end process;  
end architecture;
```


Variant 2:

```
architecture var of sigvsvar is  
    signal a : std_logic := '0';  
    signal b : std_logic := '1';  
begin  
    process  
        variable c : std_logic := '0';  
    begin  
        wait for 5 ns;  
        c := a xor b;  
        b <= a xor c;  
        wait for 5 ns;  
        c := a xor b;  
        b <= a xor c;  
        wait;  
    end process;  
end architecture;
```

- (a) Draw the waveform that you expect for the signals a and b for either implementation.
- (b) Compare your assumption with the waveforms produced by simulation.

 Problem 2

- Design a full adder implementing an **entity** FA with the appropriate input and output ports. Let the computation of all combinational outputs take 5 ns.
- Create a ripple-carry adder implementation, which instantiates full adders as **components** to form a binary word adder:



Provide a generic parameter to specify the operand width of an individual instance.

- Instantiate a ripple-carry adder adding two 4-bit words in a testbench. Provide appropriate input stimuli to validate its correct operation.
- Within your testbench, find those stimuli, which maximize the time between changing input operands and the completion of the computation. What maximum delay were you able to observe?

Problem 3 Assume the following type declaration:

```
type tFaRes is record
    c : std_logic; — Carry Bit
    s : std_logic; — Sum Bit
end record;
```

- Implement a **function** fa(a, b, c : std_logic) **return** tFaRes so that it models the operation of a full adder.
- Use this function in an alternative ripple-carry adder design, which uses a loop within a process to implement binary word addition.
Note: Do not try to enforce any explicit timing.
- Validate the correctness of this ripple-carry adder implementation using your testbench from the previous problem.